

**U.G. 1st Semester Examination - 2020**

**COMPUTER SCIENCE**

**[HONOURS]**

**Course Code : Com.Sc-H-CC-L-T-102**

**(Digital System Design)**

Full Marks : 60 Time : 2½ Hours

*The figures in the right-hand margin indicate marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**GROUP-A**

1. Answer any **ten** questions: 2×10=20
- a) What are the advantages and disadvantages of synchronous over asynchronous counter?
  - b) What do you mean by parity check?
  - c) Write the truth table of 4:1 Mux.
  - d) Simplify  $F = AB + (AC)' + AB'C(AB + C)$ .
  - e) Implement two-input NOR function using NAND gates.
  - f) Why D/A converter is useful?
  - g) What are the limitations of the Karnaugh Map?

*[Turn over]*

- h) Define setup time.
- i) State the advantages of edge triggering.
- j) State the excitation table of J-K flip-flop.
- k) Write the applications of shift registers.
- l) What is meant by tri-state logic?
- m) Differentiate between level triggering and edge triggering.
- n) Mention the classification of Integrated Circuits.
- o) Define noise margin.

**GROUP-B**

- Answer any **four** questions: 5×4=20
- 2. How will you build a 16-input MUX using only 4-input MUX? Draw and explain.
  - 3. Explain the working of 3-bit Synchronous up counter with necessary waveform and truth table.
  - 4. Explain the working of positive edge-triggered D flip-flop with the help of a logic diagram.
  - 5. a) Design an octal to binary encoder circuit with proper explanation.  
b) What is Fan out? 4+1

6. Implement the following functions:

$$F(A,B,C,D) = \sum m(1,4,8,13)$$

$$F(A,B,C,D) = \sum m(2,8,14,15)$$

using two 74183 (3 to 8 ) decoders.

7. Explain the working principle of 7477 BCD to 7-segment LED decoder.

### GROUP-C

Answer any **two** questions: 10×2=20

8. a) Design a Combinational circuit to output the 2's complement of a 4-bit binary number.

b) Design a full adder using 2-input NAND gates only. 6+4

9. a) Design a logic circuit that has 4 inputs, the output will only be high when at least two adjacent bits are same.

b) Implement the function


$$F(A, B, C) = \sum (1, 2, 5, 7)$$

using 4 to 1 MUX. 6+4

10. a) Explain the working principle of 4-bit binary ripple counter with the help of logic diagram and truth table.

b) Design a 3-bit even parity generator circuit. 6+4

 11. a) Analyse the following sequential circuit and obtain excitation, transition and state tables. Draw the state transition diagram for the same.



b) Define race condition. 8+2

\_\_\_\_\_