

**U.G. 1st Semester Examination - 2019****COMPUTER SCIENCE****[HONOURS]****Course Code : Com.Sc(H)CCL-102-T**

Full Marks : 60

Time : 2½ Hours

*The figures in the right-hand margin indicate marks.**Candidates are required to give their answers in their own words as far as practicable.***GROUP-A**

1. Answer any ten questions: 2×10=20
- a) What is Duty cycle?
  - b) Write the difference between Latch and Flip-Flop.
  - c) Define Gray code.
  - d) Why D/A converter is useful?
  - e) Simplify  $F=BC+BC'+BA$
  - f) Write down the significance of preset input in flip-flop.
  - g) State Consensus Law of Boolean algebra.
  - h) Define LSI.

*[Turn over]*

- i) Why encoders are useful?
- j) State the excitation table of S-R flip-flop.
- k) Expand  $F=x+y z$  into minterms.
- l) What do you mean by edge triggering?
- m) Why NOR is called universal gate?
- n) Why any Boolean function can be designed by using decoder?
- o) How XOR can be used as NOT gate?

### GROUP-B

Answer any **four** questions:

5×4=20

- 2. Draw and explain 3-input AND gate using Diode.
- 3. Design and implement Full subtractor using full adder.
- 4. a) Implement, with a decoder and external OR gates, the combinational circuit specified by the following two Boolean functions
  - i)  $f_2(A, B, C) = \sum m(1, 2, 7)$
  - ii)  $f_3(A, B, C) = \prod M(0, 1, 2, 4)$
- b) What is Fan out? (2+2)+1

5. Implement the following function using 8:1 MUX along with explanation

$$F(A, B, C, D) = \Sigma m(0, 2, 6, 10, 11, 12, 13) + d(3, 8, 14)$$

6. Explain the working principle of J-K master slave flip-flop with circuit diagram along with waveform.
7. Design a three input A, B, C and one output Y circuit; minimal, two level gate combinational circuit which has an output equal to 'zero' when majority of its input are at logic '1'.


### GROUP-C

Answer any two questions:

10×2=20

8. a) Convert D flip-flop to J-K flip-flop.
- b) Design a 1-bit comparator using 2-4 decoder giving 3 outputs G, E, L. 6+4
9. a) Explain race around condition.
- b) Design and describe asynchronous Decade Counter using J-K flip-flop. Draw the timing diagram also. 2+(6+2)

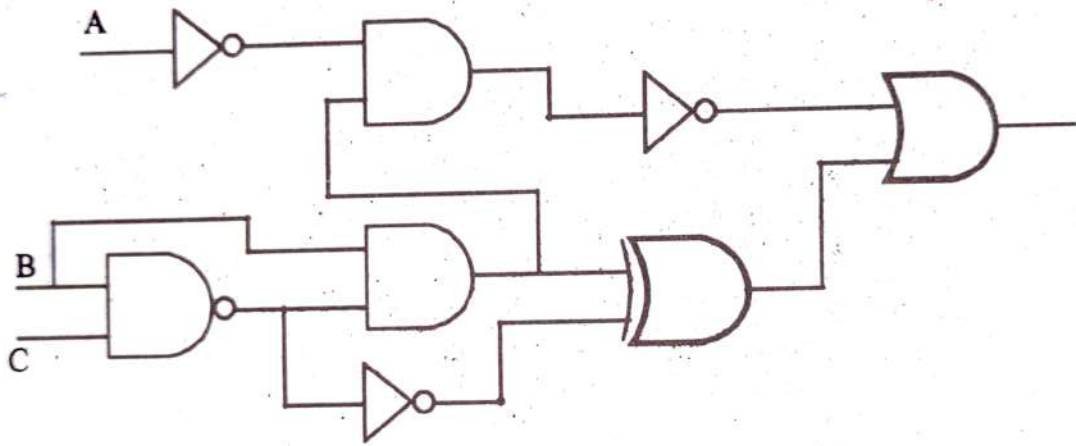10. a) Write a short note on parallel adder.
- b) Simplify the following function. Also find out prime implicants and essential prime implicants:  
 $F(W, X, Y, Z) = \Sigma m(2, 3, 5, 7, 10, 11, 13, 14, 15)$   
 $4+(4+1+1)$
11. a) What will be the expression of Y for the following diagram.



Also draw the truth table for the same.

- b) Using a suitable decoder, design a circuit which will detect even no. of 1's in a 4-bit binary number.  $(2+3)+5$